## 

DETAILED DESCRIPTION

Cir- cuit	Unit.	General Description.	Power.		
Sym- bol.			5 w.	50 w.	250 w.
$\stackrel{L_{ m o}}{C_{ m o}}$	Antenna inductor				
$C_{\rm o}$	Antenna series con- denser	$ \begin{cases} .0003 \text{ to} \\ .003 \text{ mfd.} \end{cases} $	8000 v.	8000 v.	8000 v.
$\frac{L_{\mathrm{p}}}{C_{\mathrm{p}}}$	Plate coupling coil Plate tuning condenser	4" dia.	30 t.	30 t.	30 t.
$C_{ m p}$	Plate tuning condenser	variable, 0005 mfd.	500 v.	1500 v.	3000 v.
$C_1$	Grid condenser	.002 mfd.	1500 v.	1500 v.	1500 v.
$R_1$	Grid resistance	5000 to 10,000 ohms			
X	R.F. choke-coil	see Art. 44 (d)			
C	Oscillating circuit con-	.001 mfd.	2000 v.	4000 v.	8000 v.
$L_2$	denser Oscillating circuit plate	.but ind.	2000 γ.	4000 V.	8000 V.
_	coil	6" dia.	7	9	10
$L_1$	Oscillating circuit grid	6" dia.	7	5	4
$R_2$	Filament rheostat		2 a.	8 a.	16 a.
A	Antenna ammeter		2 a.	4 a.	8 a.

*Note.*—The construction of coils  $L_1$  and  $L_2$  is the same as that of the antenna inductor  $L_0$ . (See Art. 44 (a).)

## CIRCUIT NO. 7

## MASTER-OSCILLATOR ARRANGEMENT

This circuit is adapted for use with either direct ground or counterpoise. or with any combination of direct grounds and counterpoises by the method of Art. 26. The condenser  $C_n$  is a convenience for tuning and may be omitted if desired. An inductance of approximately 60 micro-henries will be required in  $L_{\rm p}$  for any of the three types of tubes used singly, with an antenna resistance of 15 ohms at wavelengths from 200 to 300 meters and an oscillator efficiency of 50 per cent. The choke-coil X serves to reduce the grid loss by preventing the flow of radio frequency currents through the biasing resistance  $R_1$ . The master oscillator employs the Hartley circuit with two coils  $L_1$ and  $L_2$  shunted by a condenser C. This condenser may be made variable for convenience, or should at least be shunted by a variable condenser if precise adjustment of the wavelength is to be made. The coils  $L_1$  and  $L_2$  are constructed in the same way as the antenna coil as described in Art. 44 (d). For the excitation of the 5, 50 and 250-watt tubes the master-oscillator tube should be an overloaded receiving tube with 300 volts or so on its plate. capable of supplying 0.2 watt, a 5-watt tube, and a 50-watt tube in the respective cases. For a general discussion of this circuit and instructions for its adjustment see Art. 48.